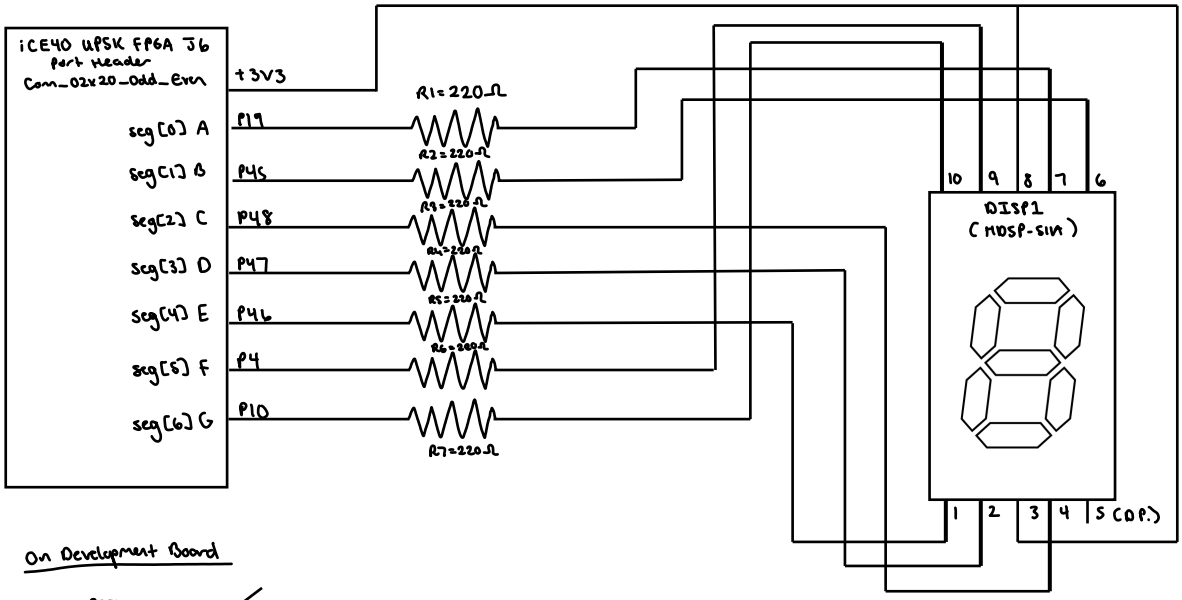
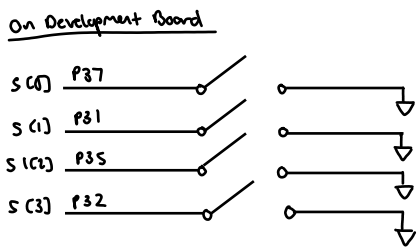
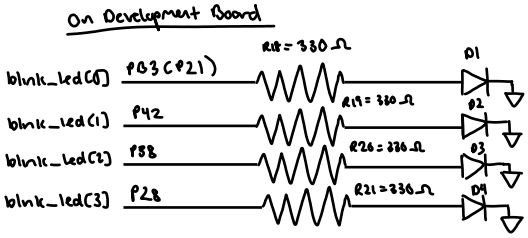






7-Segment Display

Author: Tiffany Nguyen | 9/20/26

Referring to E155 Development Board schematic, the on-board DIP switch S[3:0] and LEDs blink_led[3:0] are found under SW6 and the series of LEDs, respectively. FPGA pins are those not in the PAXX or PBXX form.

https://hmc-e155.github.io/assets/doc/E155%20FA22%20Development%20Board%20Schematic.pdf